

Task 1.2

Design D flip flop using logic gates

